

Alternating power supply

(parameters, L , C and R)



***a.c.* circuits**

Parameters of *a.c.* circuits

R , C and L connected to *a.c.*

Phasor & series combinations

Power and Power factor

Resonance and quality factor

L-C oscillations

Transformer

Comparison of *d.c.* and *a.c.*

***d.c.* power supply**

- ☐ Polarity of terminals is retained
- ☐ Magnitude and direction of potential difference remains constant (in steady state)
- ☐ Magnitude and direction of current remains constant (in steady state)
- ☐ Relatively difficult to generate and convert



***a.c.* power supply**

- ☐ Polarity of terminals is not retained
- ☐ Magnitude and direction of potential difference varies periodically with time
- ☐ Magnitude and direction of current varies periodically with time
- ☐ Relatively easy to generate and convert



Power supply in a.c. and the equation

Potential difference across the terminals of an a.c. power supply varies periodically as a function of time.

Instantaneous voltage

$$V = V_o \sin(\omega t)$$


Peak voltage

Angular frequency

time

Note :

$$\omega = 2\pi n = \frac{2\pi}{T}$$

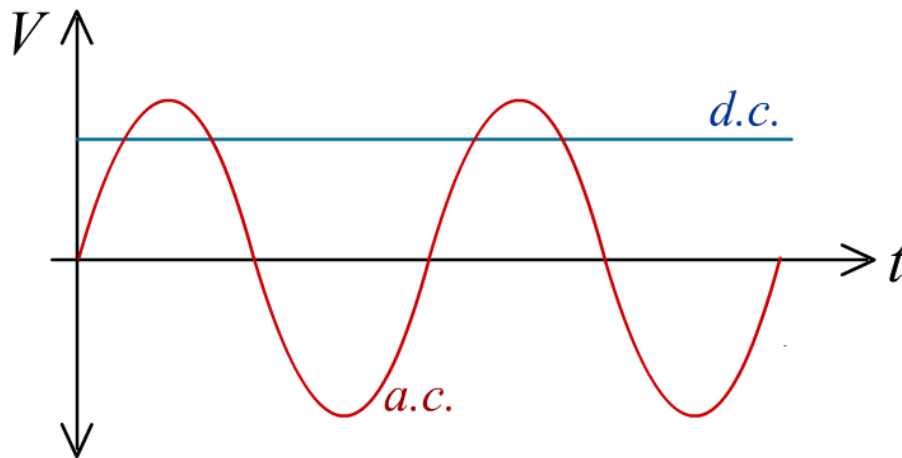


Power socket that you see near you gives a.c.

rms values

rms value: root of mean of square of the value

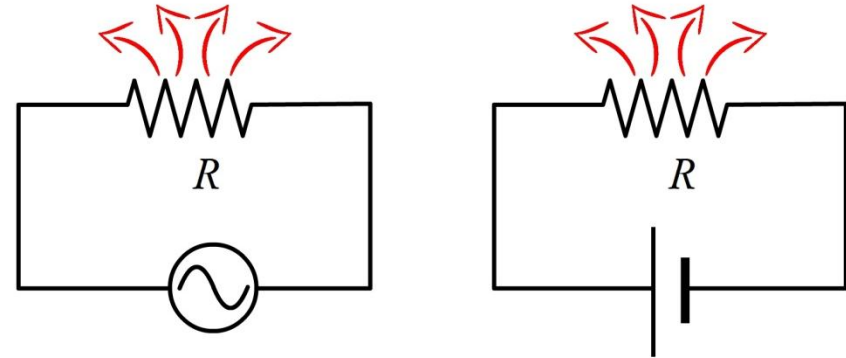
For a peak current I_o of an *a.c.* passing through a resistor, the effective value of *d.c.* current that results in the same dissipation of heat (as in case of *a.c.*) through the resistor is called *rms* value of the *a.c.*



For a pure sinusoidal *a.c.*, *rms* values of current and voltage are related to their peak values as

$$V_{\text{rms}} = \frac{V_o}{\sqrt{2}}$$
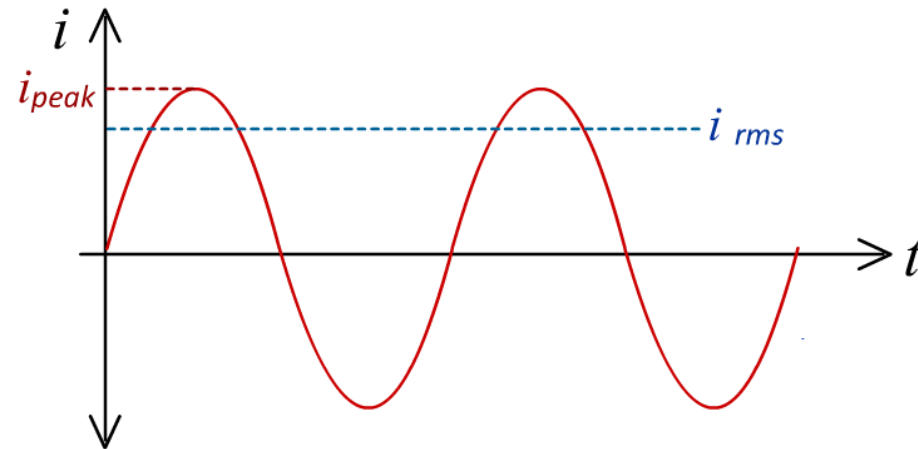
$$I_{\text{rms}} = \frac{I_o}{\sqrt{2}}$$



Note : rms value is also called effective value

[Click here for simulation](#)

***a.c.* circuits**

A note of what we will do (for a major part) in this chapter

We study the phenomenon resulting from connecting the following three circuit elements to an *a.c.* power supply.

- (a) Resistor (R) It always opposes current, no matter what
- (b) Inductor (L) It opposes change in current, (but not constant current !)
- (c) Capacitor (C) It 'dances' to the tune of an *a.c.*

In each case we look at

- (a) Variation of current (i) as a function of time
- (b) Net opposition called impedance (Z) to flow of current
- (c) Peak value of current (i_o)
- (d) Phase difference (ϕ) between current and applied potential
- (e) Average power dissipated in each cycle of the *a.c.* source

Resistor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — i

Using Kirchhoff's loop law we get

$$V_o \sin(\omega t) - iR = 0$$


$$iR = V_o \sin(\omega t)$$

$$i = \frac{V_o}{R} \sin(\omega t)$$

$$i = i_o \sin(\omega t) \text{ — } \text{ii}$$

where
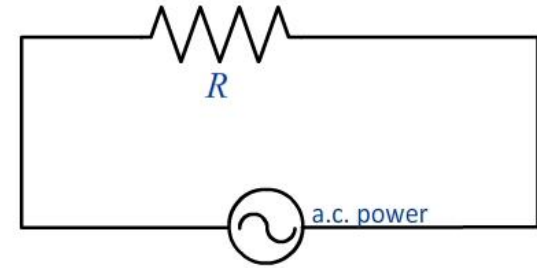
$$i_o = \frac{V_o}{R} \text{ — } \text{iii}$$



- ☐ Current is in phase with voltage
- ☐ Peak current is directly proportional to applied voltage and inversely proportional to resistance
- ☐ Peak current is independent of frequency of a.c.
- ☐ Impedance in the circuit is due to R
- ☐ Impedance is independent of frequency of power supply

Resistor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — i



$i = i_o \sin(\omega t)$ — ii

$i_o = \frac{V_o}{R}$ — iii



Resistance is independent of frequency of a.c. power supply

[Click here for simulation](#)

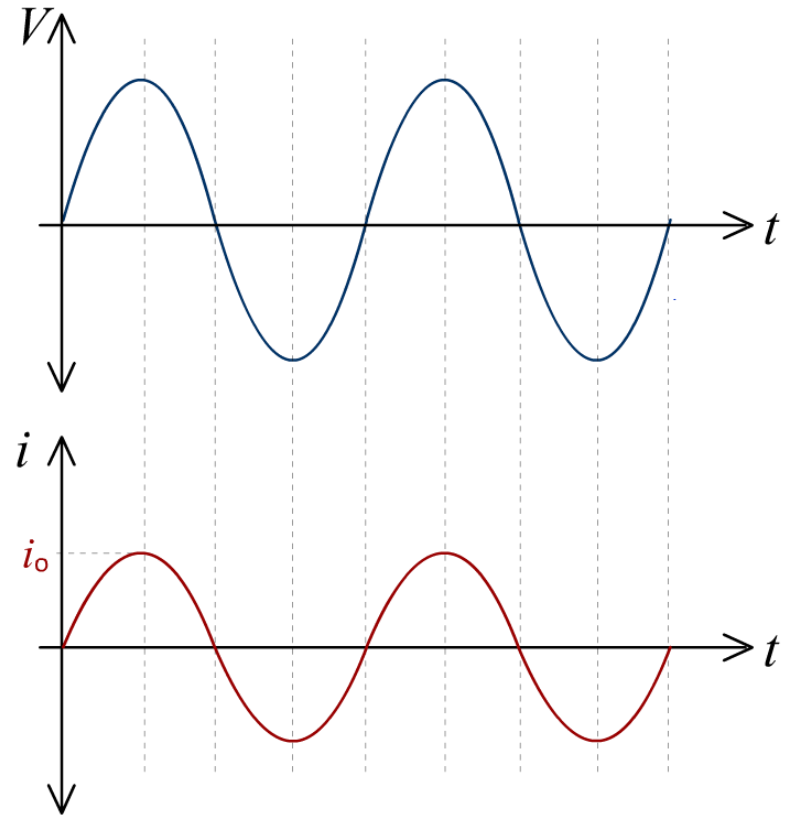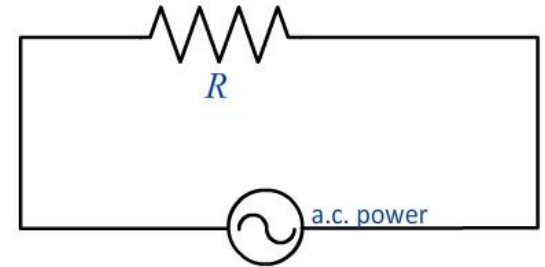

Current is in phase with voltage

Capacitor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — i

Using Kirchhoff's loop law we get

$$V_o \sin(\omega t) - \frac{q}{C} = 0$$

$$\frac{q}{C} = V_o \sin(\omega t)$$


$$q = CV_o \sin(\omega t)$$

differentiating w.r.t. time

$$\frac{dq}{dt} = CV_o \omega \cos(\omega t)$$

$$i = \frac{V_o}{1/C\omega} \sin\left(\omega t + \frac{\pi}{2}\right)$$
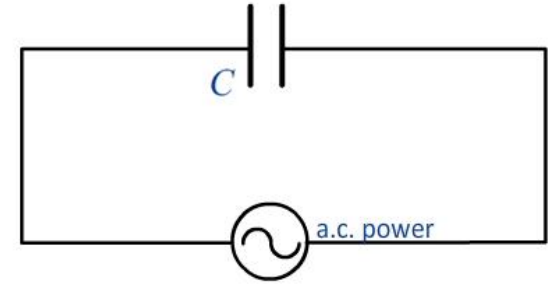
$$i = i_o \sin\left(\omega t + \frac{\pi}{2}\right)$$
 — ii



where

$$i_o = \frac{V_o}{X_c}$$
 — iii

$$X_c = \frac{1}{C\omega}$$
 — iv

- ❑ Phase difference between i and V is $\pi/2$
- ❑ Peak current is directly proportional to applied voltage and inversely proportional to capacitive reactance (X_c)
- ❑ Impedance in the circuit is due to capacitive reactance i.e. $X_c = 1/C\omega$
- ❑ X_c is inversely proportional to frequency of power supply


Capacitor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — **i**

$$i = i_o \sin\left(\omega t + \frac{\pi}{2}\right)$$
 — **ii**



$$i_o = \frac{V_o}{X_c}$$
 — **iii**

$$X_c = \frac{1}{C\omega}$$
 — **iv**

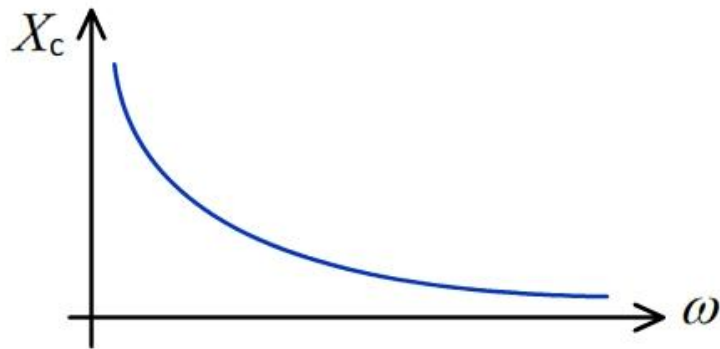

Capacitive reactance decreases with increase in frequency of a.c. power

[Click here for simulation](#)

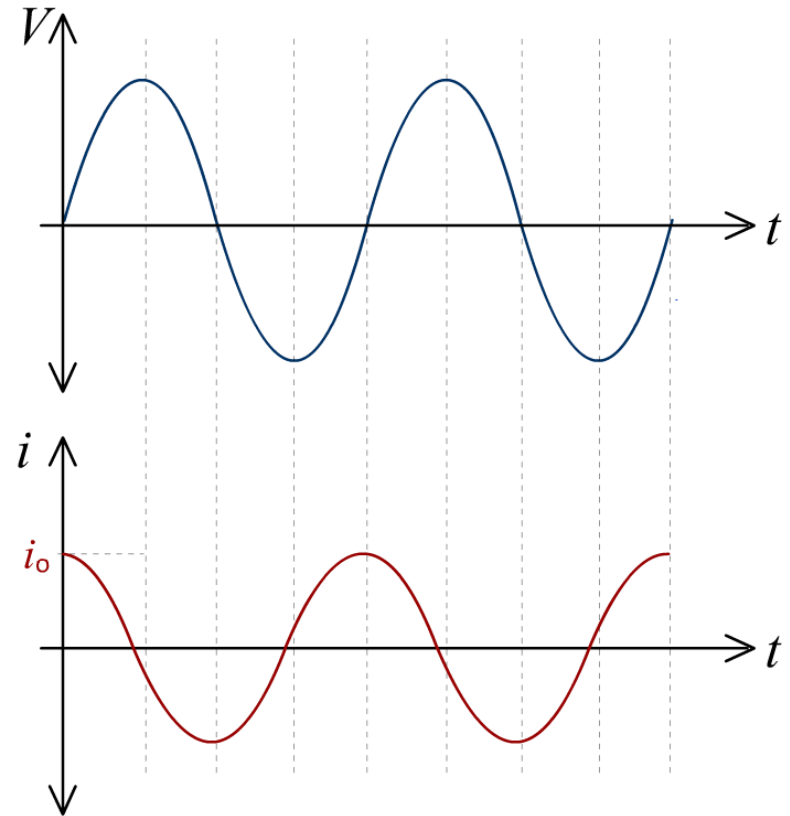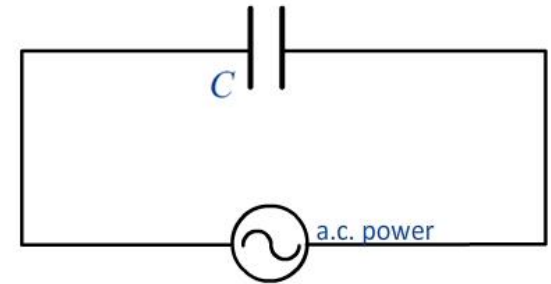

Current leads voltage by $\pi/2$

Inductor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — i

Using Kirchhoff's loop law we get

$$V_o \sin(\omega t) - L \frac{di}{dt} = 0$$


$$L \frac{di}{dt} = V_o \sin(\omega t)$$

$$di = \frac{V_o}{L} \sin(\omega t) dt$$

Integrating the above eq we get

$$i = -\frac{V_o}{L\omega} \cos(\omega t)$$
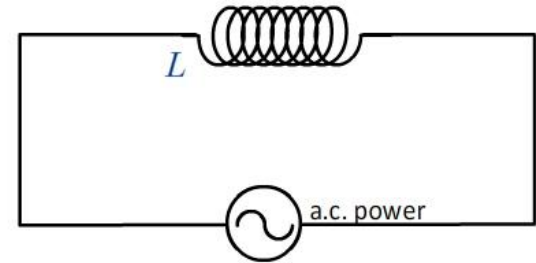
$$i = i_o \sin\left(\omega t - \frac{\pi}{2}\right)$$
 — ii



where

$$i_o = \frac{V_o}{X_L}$$
 — iii

$$X_L = L\omega$$
 — iv

- ☐ Phase difference between i and V is $-\pi/2$
- ☐ Peak current is directly proportional to applied voltage and inversely proportional to inductive reactance (X_L)
- ☐ Impedance in the circuit is due to inductive reactance i.e. $X_L = L\omega$
- ☐ X_L is directly proportional to frequency of power supply


Inductor connected to a.c. power supply

Applied voltage : $V = V_o \sin(\omega t)$ — **i**

$$i = i_o \sin\left(\omega t - \frac{\pi}{2}\right) \text{ — **ii**}$$



$$i_o = \frac{V_o}{X_L} \text{ — **iii**}$$

$$X_L = L\omega \text{ — **iv**}$$

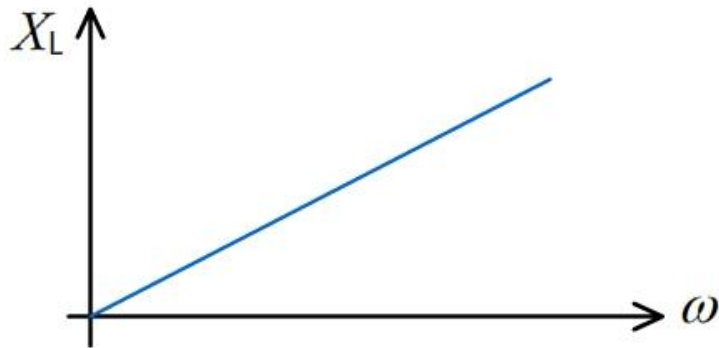

Inductive reactance increases with increase in frequency of a.c. power

[Click here for simulation](#)

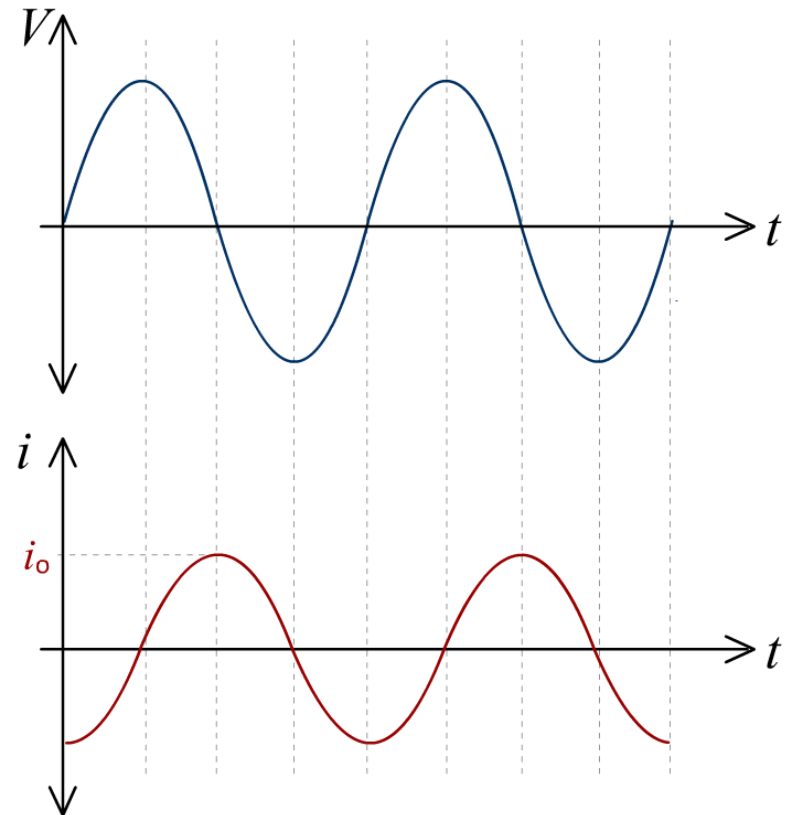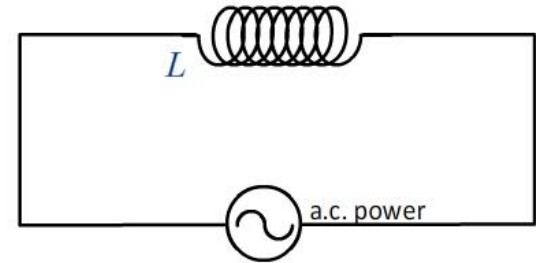

Current lags behind voltage by $\pi/2$